

Assignment

- 1) Two resistors R_1 and R_2 are connected in
 - a) a series combination b) a parallel combination
 and the combination is connected to a battery of $6V$.
 - 1) In which case will the potential difference across R_1 and R_2 be same.
 - 2) In which case will the current through R_1 and R_2 be the same.

- 2) Two conducting wires of same material, equal in length and equal diameter are first connected in series and then in parallel. Compare the equivalent resistance in each case.

- 3) Two metallic wires A and B are connected in parallel. Wire A has length l and radius r , wire B has a length $2l$ and radius r . Compare the ratio of the total resistance of parallel combination and the resistance of wire A? (both the wires are made of the same material)

- 4) How does the increase in temperature affect the resistance of a) conductor b) insulator

- 5) Name the device used for the ch. to change the resistance of a circuit

- 6) What does the slope of a $V-I$ graph represent.


- 7) Slope are Ohm.

- 8) What is electrical resistivity? How does it depend on temperature? What is its S.I unit?


to form the sides of a rhombus ABCD. Calculate the total resistance and total current if a battery of 5V is connected across A and C.

10) What is the difference between resistance and resistivity.

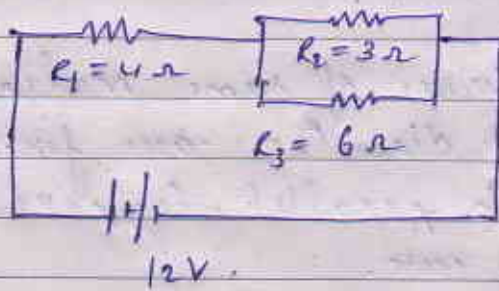11) In the given circuit find i) total current.
ii) total resistance. iii) voltage across R_1 .



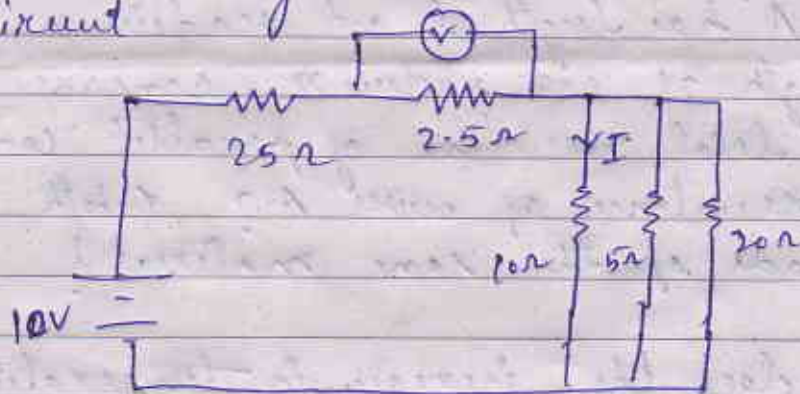12) Find the voltage V and current I in the given circuit.



13) Forty electric bulbs are connected in series with the mains of 220V. After one bulb is fused, a) what will happen to the remaining bulbs.

b) are again connected

b) If the remaining bulbs are once again connected in series across the same main what will be the effect on illumination?

14) NCERT exercise questions Pg 221.

1, 3, 7, 8, 13, 16, 18